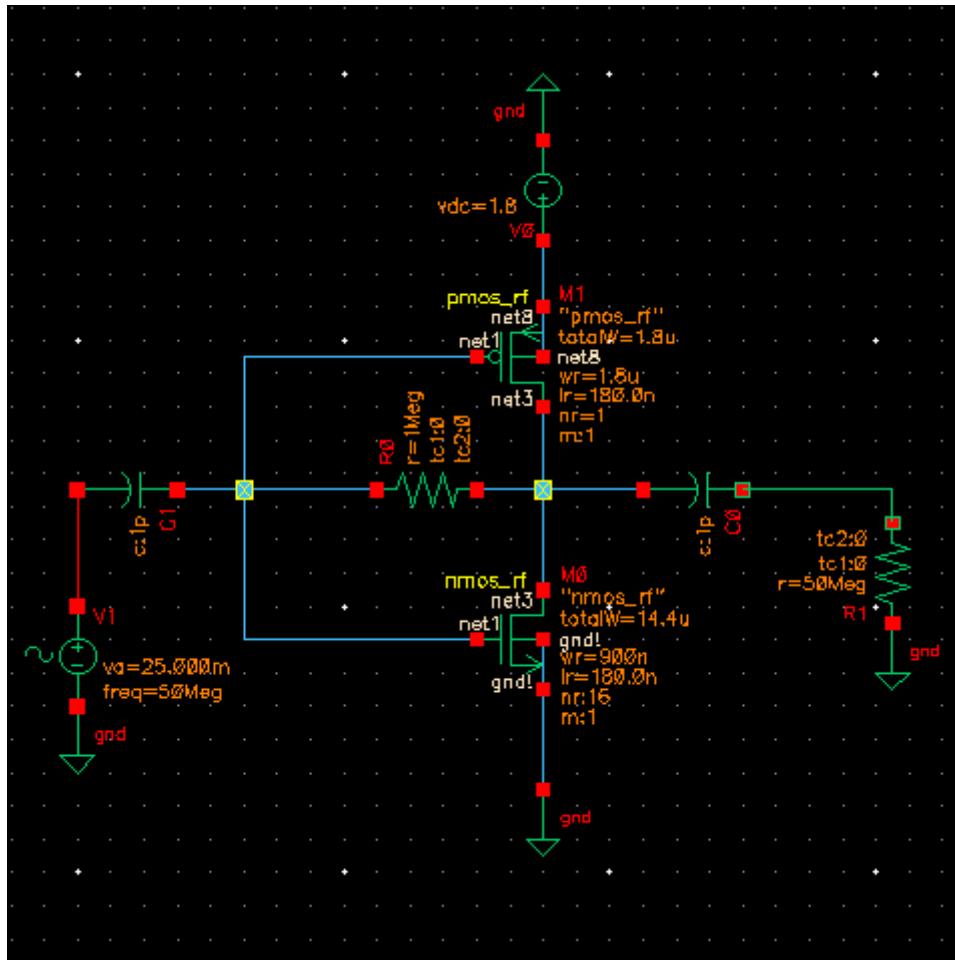


AIC ASSIGNMENT-1

Q2)

a)

- Below is the figure corresponding to the netlist given by the code q2_2022.cir



b)

TABLE-1: Harmonics for small signal input 0.025

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.462722	-178.75	1
2	1x10 ⁸	0.00997123	91.27	0.0216
3	1.5x10 ⁸	0.01181	179.30	0.025514

TABLE-2: Harmonics for small signal input 0.010

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.197107	-178.65	1
2	1x10 ⁸	0.00252278	90.8191	0.012799
3	1.5x10 ⁸	0.00657743	179.064	0.00333698

TABLE-3: Harmonics for small signal input 0.030

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.535191	-178.81	1
2	1x10 ⁸	0.00989873	91.2788	0.0184957
3	1.5x10 ⁸	0.02121	179.497	0.0396307

TABLE-4: Harmonics for little large signal input 0.035

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.596783	-178.89	1
2	1x10 ⁸	0.00765952	90.9273	0.0128347
3	1.5x10 ⁸	0.0341138	179.717	0.0571628

TABLE-5: Harmonics for little large signal input 0.05

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.722821	-179.19	1
2	1x10 ⁸	0.00261846	-82.629	0.00362257
3	1.5x10 ⁸	0.08308	179.955	0.114881


TABLE-6: Harmonics for little large signal input 0.06

HARMICS	FREQUENCY	MAGNITUDE	PHASE	NORMALISED MAGNITUDE
1	5x10 ⁷	0.775711	-179.39	1
2	1x10 ⁸	0.00803783	-82.361	0.0103619
3	1.5x10 ⁸	0.112825	179.794	0.145447

c)

- At an input voltage of **45.68mV** the THD value from the netlist is coming closer to 10% which is **THD=10.0009 %**,

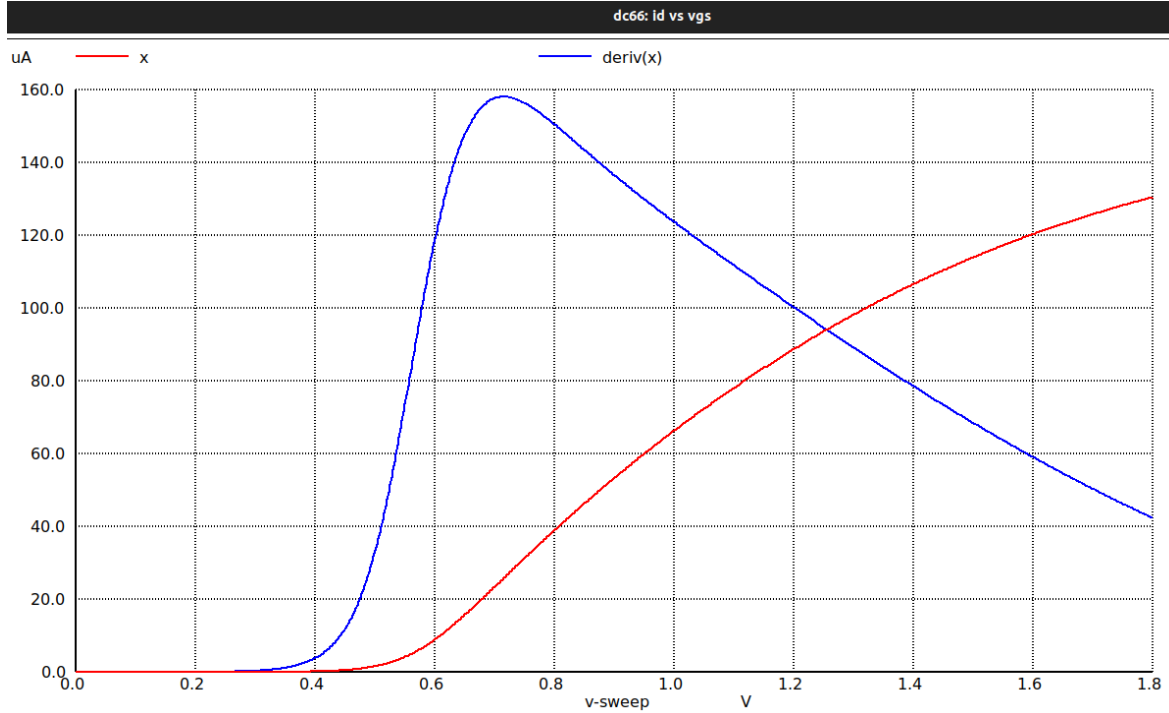- At an input voltage of **83.13mV** the THD value from the netlist is coming closer to 20% which is **THD=20 %**,




d)

- To increase the linearity we can decrease the gain by changing the VG bias shift or we can decrease the length of the mosfets we use. By this I changed the lengths of the mosfets in the netlist to the value of 0.09um so that the gain will be lower but by looking into the THD of the voltages in the c part are dropped. Below the THD values are shown for the process we proceeded above
- At an input voltage of 45.68mV the THD value from the netlist is coming closer to **THD=1.12623 %**,
- At an input voltage of 83.13mV the THD value from the netlist is coming closer to **THD=5.58003%**,

Q3)

a)

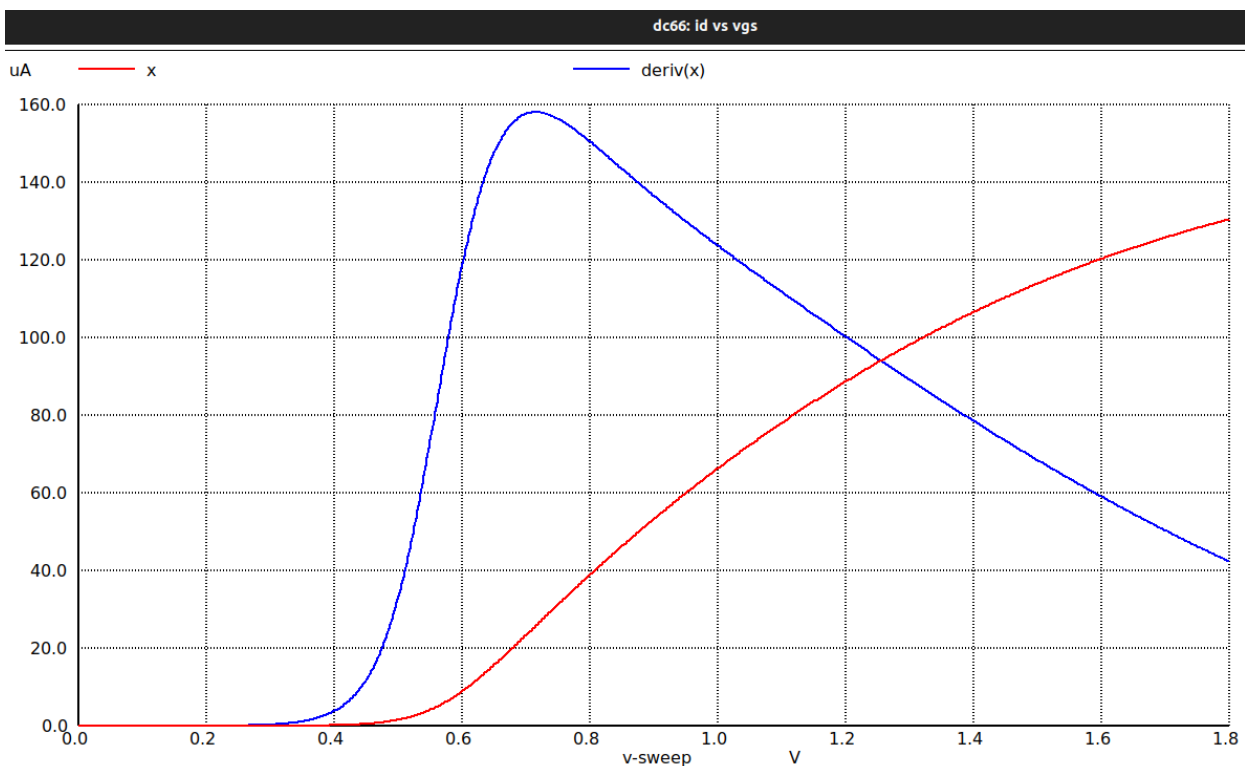

- In above plot X is the current I_d flown with respect to the sweep V_{GS} from 0-1.8 with step 0.1.
- As discussed in the class effect on μ that is if we increase V_{GS} more the μ which implies mobility of the charges. So now


$$\mu' = \frac{\mu}{1 + \theta(V_{GS} - V_T)} \quad (1)$$

- Now as observing that the

$$I_d = \alpha(V_{GS} - V_T) \quad (2)$$

- Alpha contains the mobility factor μ so the effect will not be seen in the place where the slope alpha is max we found that point and drawn a straight line from that point and found the x-intercept which is indefinitely named as threshold voltage
- comes to calculations the slope is highest at **$I_d = 2.45946 \times 10^{-5} A$ $V_{GS} = 0.712264 V$ slope is 158×10^{-6}**
- taking above values into considerations and calculating the x-intercept we got threshold voltage V_T as **0.5566**

b)

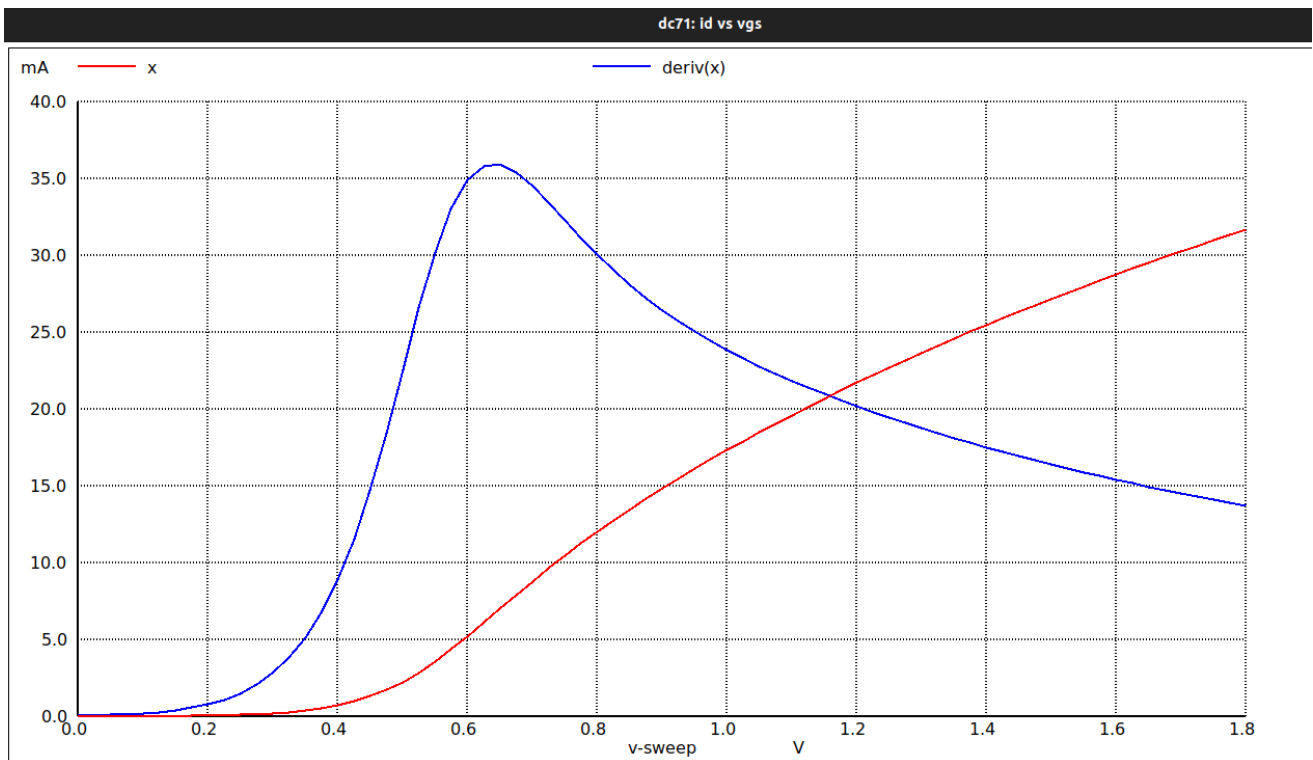

- Here Given V_{DS} is 1.8 $V_{GS} - V_T$ will always be less than V_{DS} so the mosfet will always be in saturation mode so I_d is given by equation below

$$I_d = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \quad (3)$$

- Now we are interested in finding V_T so i want to linearise the $V_{GS} - V_T$ so i wanted to plot $\sqrt{I_d}$ vs V_{GS} curve which will be linear the above discussed change in carrier mobility should be considered in this case also
- So as from above point we will find the x-intercept for the straight line plotted at the highest slope point in $\sqrt{I_d}$ vs V_{GS}
- comes to calculations the slope is highest at **$\sqrt{I_d} = 0.0628378$ $V_{GS} = 0.638393 V$ slope is 0.0361486**
- From above values obtained from ng-spice $V_{threshold}$ is given by **$V_T = 0.4646 V$**

c)

- As Observed the value of threshold voltage is higher in the first case than the second case, as in first case the mosfet is in a triode state but in the case of b part the mosfet is in saturation region, as velocity of carriers is saturated the threshold voltage will be dropped and below is the expression for new threshold voltage(DIBL)
- in case a DIBL will not be effective as it is in triode state but as in part b the mosfet in saturated state so DIBL is effective

$$V_T' = V_T - \eta V_{DS} \quad (4)$$

d)

- We have the maximum slope point from the part B from that we can find the μ_{Cox} the value is approximately equal to 2.614×10^{-4}


e)

$$I_d = I_0 e^{\frac{V_{GS}}{\eta V_{thermal}}} \quad (5)$$


- Apply logarithm on both sides

$$\log(I_d) = \log(I_0) + \frac{V_{GS}}{\eta V_{thermal}} \quad (6)$$

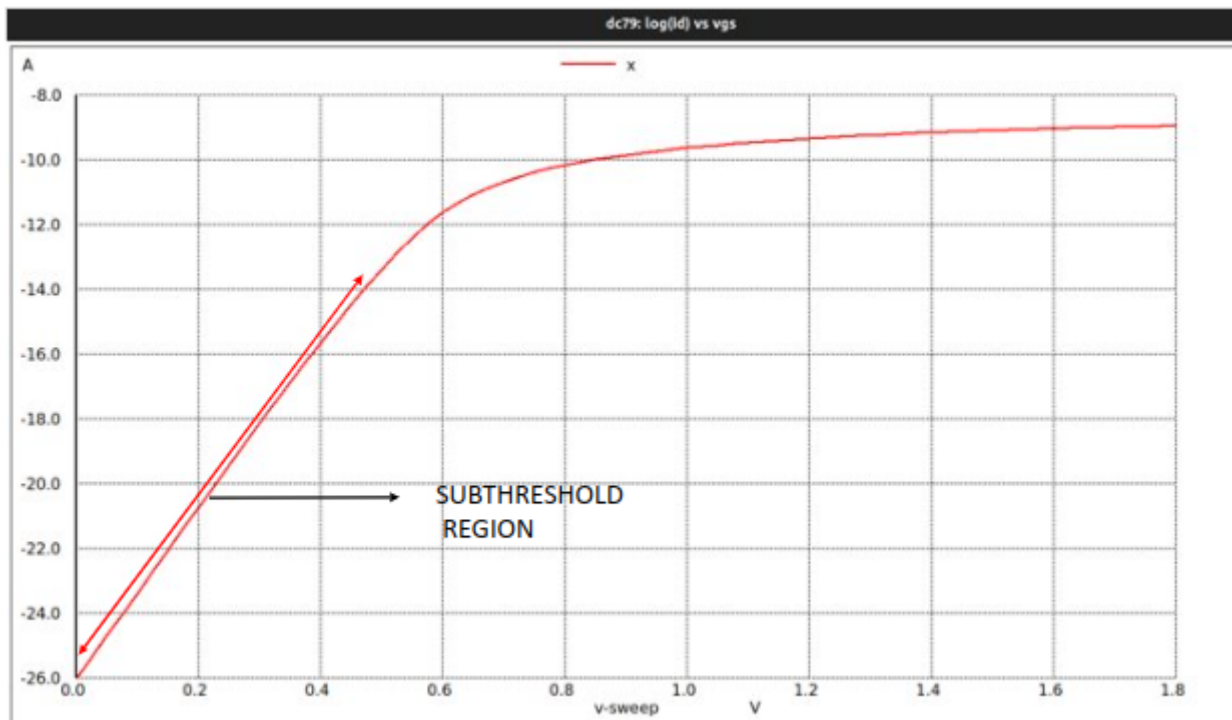- by looking into above equation and plot we got from either of the parts we can calculate η
- $\log(I_d)$ vs V_{GS} for $V_{DS} = 50mV$



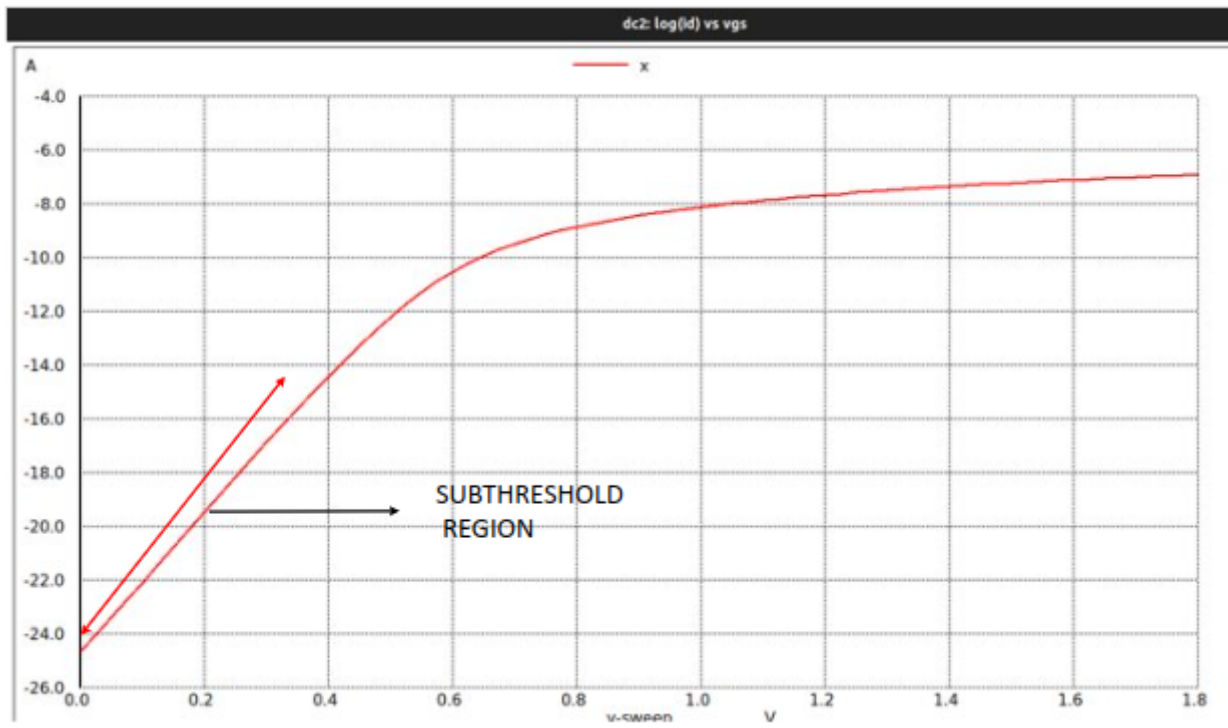- On calculation by taking a value at $V_{GS} = 0.3V$ we got $\eta = 1.4875$
- $\log(I_d)$ vs V_{GS} for $V_{DS} = 1.8V$



- On calculation by taking a value at $V_{GS}=0.3$ V we got $\eta = 1.4815$